

july 2016

8. Calculate EACH of the following for a 100 W, 250 V electric filament lamp:
- (a) The operating resistance; (4)
 - (b) The operating current. (3)

Q7 July 2015

An electric fire operated from a 240V supply has a heating element comprising two 30Ω coils. The coils may be wired in series to give a low setting or in parallel to give a high setting. Calculate EACH of the following:

- (a) The power output of the low setting. (5)
- (b) The power output of the high setting. (5)

dec 2014

7. A 6 ohm resistor is connected in parallel with a 3 ohm resistor, and this combination is connected in series with a 4 ohm resistor. The applied voltage is 12 volts.

Calculate EACH of the following:


- (a) the total current in the circuit; (4)
- (b) the power dissipated by EACH component. (6)

Q7 July 2015

An electric fire operated from a 240V supply has a heating element comprising two 30Ω coils. The coils may be wired in series to give a low setting or in parallel to give a high setting. Calculate EACH of the following:

- (a) The power output of the low setting. (5)
- (b) The power output of the high setting. (5)

a)

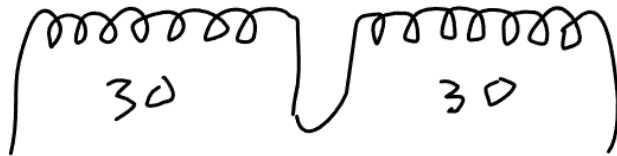

$$R_T = R_1 + R_2$$

$$R_T = 30 + 30 = 60\Omega$$

$$P = 4 \times 240 = 960W$$

$$P = IV$$




$$V = 240$$

I

$$R = 60$$

$$I = \frac{V}{R}$$

$$I = \frac{240}{60} = 4$$

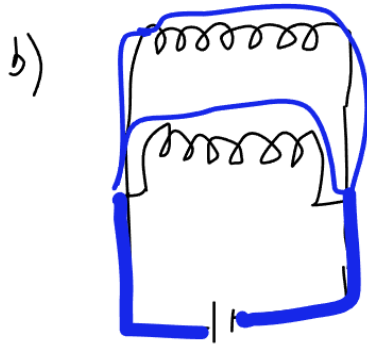

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{30} + \frac{1}{30}$$

$$\frac{2}{30}$$

$$\frac{1}{R_T} = \frac{1}{15}$$

$$R_T = 15 \Omega$$

$$V = 240$$
$$R = 15$$
$$I = \frac{V}{R} = \frac{240}{15} = 16 \text{ Amps}$$

$$P = 1 \text{ V}$$

$$P = 16 \times 240 = 3.84 \text{ kW}$$

july 2016

8. Calculate EACH of the following for a 100 W, 250 V electric filament lamp:

(a) The operating resistance; (4)

(b) The operating current. (3)

$$P = I V$$



$$100 = 250 I$$

$$I = \frac{100}{250}$$

$$\underline{I} = 0.4 \text{ A}$$


$$R = \frac{250}{0.4} = 625 \Omega$$

dec 2014

7. A 6 ohm resistor is connected in parallel with a 3 ohm resistor, and this combination is connected in series with a 4 ohm resistor. The applied voltage is 12 volts.

Calculate EACH of the following:

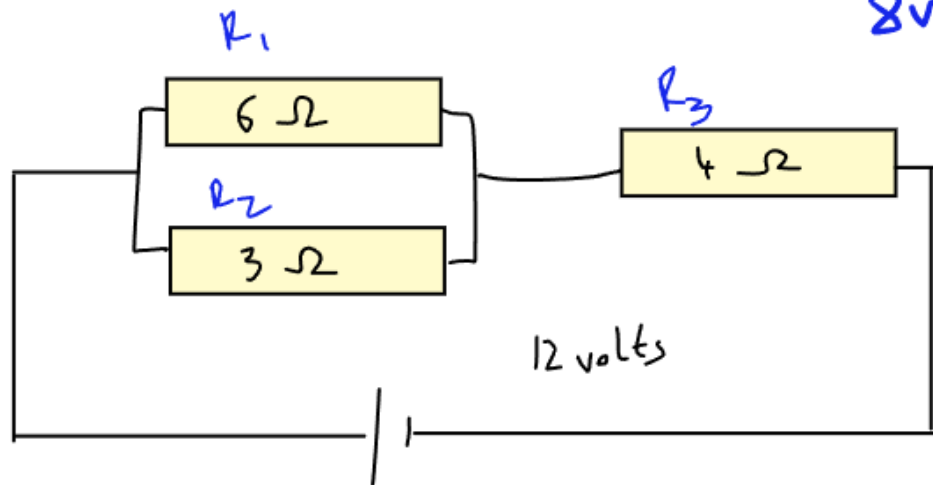- (a) the total current in the circuit; (4)
- (b) the power dissipated by EACH component. (6)




8 volts Parallel Resistors

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{6} + \frac{1}{3}$$

$$\frac{1}{R_T} = \frac{1}{2}$$

$$R_T = 2\Omega$$

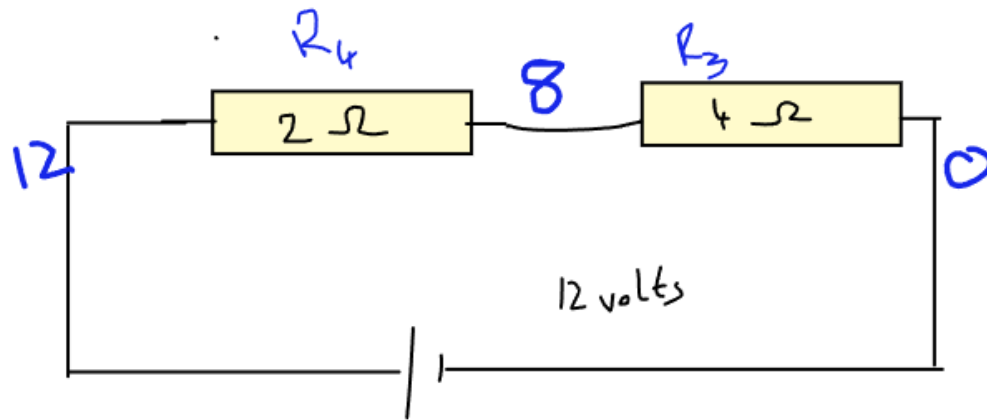


Series Resistors

$$R_T = R_4 + R_3$$

$$6 = 2 + 4$$

$$R_T = 6 \Omega$$

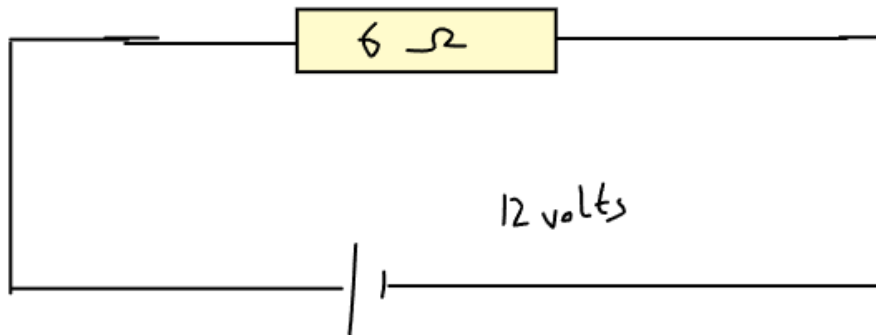

Circuit

$$V = 12$$



$$I = 2 \text{ Amp}$$

$$R = 6$$



$$I = \frac{12}{6} = 2 \text{ Amps}$$

$$P = IV$$
$$I = 2$$

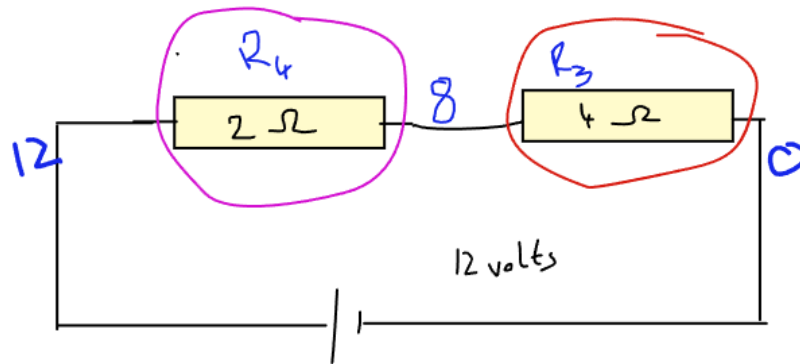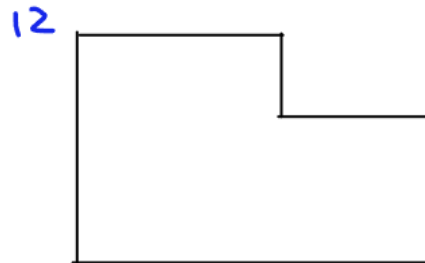

Voltage drop over R_4



$$V$$
$$I = 2$$
$$R = 2$$

$$V = 2 \times 2 = 4 \text{ Volts}$$

Voltage drop over R_3

$$V = 8$$


$$I = 2$$


$$R = 4$$

$$V = 2 \times 4 = 8 \text{ volt}$$

$$P = IV$$

$$P_3 = 2 \times 8 = 16 \text{ watts}$$

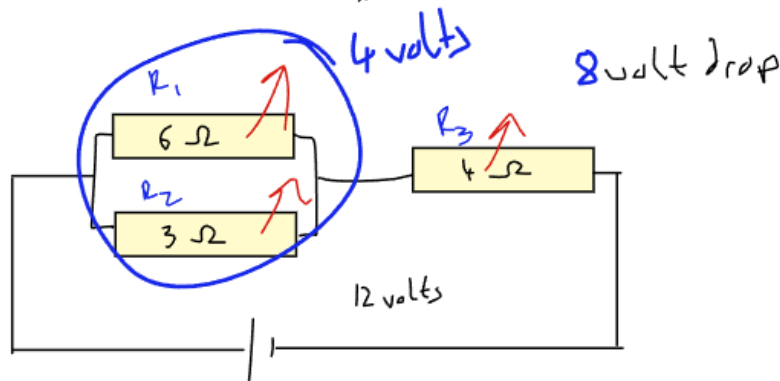

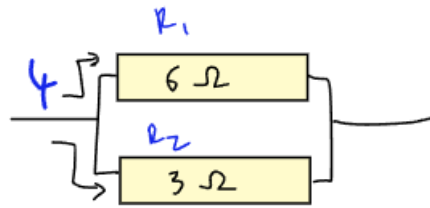

Supply Voltage = 4 V
 $V = 4$



R_1
 $V = 4$
 $R = 6$

I
 $I = \frac{V}{R} = \frac{4}{6} = \frac{2}{3} \text{ Amp}$

$P = IV$
 $P = \frac{2}{3} \times 4$

$P_1 = 2.6667 \text{ Watts}$

R_2
 $V = 4$
 $R = 3$
 I

$I = \frac{V}{R} = \frac{4}{3} \text{ Amp}$

$P = IV$

$P = \frac{4}{3} \times 4$

$P_2 = 5.3333 \text{ Watts}$