

Q8 March 2018

A 4 Ohm resistor is connected in parallel with a 6 Ohm resistor, and this combination is connected in series with an 8 Ohm resistor. The current flowing through the 8 Ohm resistor is 7.5 Amps. Calculate EACH of the following:

- (a) The applied voltage; (4)
- (b) The current in EACH of the parallel resistors. (4)

Q9 December 2019

A battery has an e.m.f. of 38 volts and an internal resistance of 4 ohms. It feeds a circuit consisting of three resistors connected in parallel. The resistors have values of 10 ohm, 20 ohm and 30 ohm.

Calculate EACH of the following:

- (a) the battery terminal voltage; (4)

- (b) the current in EACH resistor.

Q9 March 2017

A battery consists of 10 cells connected in series, each cell having an e.m.f. of 2V and an internal resistance of 0.05Ω . The battery supplies a current of 5A to an electric motor.


Calculate each of the following:

- (a) the potential difference of the battery; (5)
- (b) the resistance of the electric motor. (3)


Q8 December 2016

A battery of EMF 12V and internal resistance 0.2Ω is connected across the terminals XY of the circuit shown. Calculate EACH of the following:

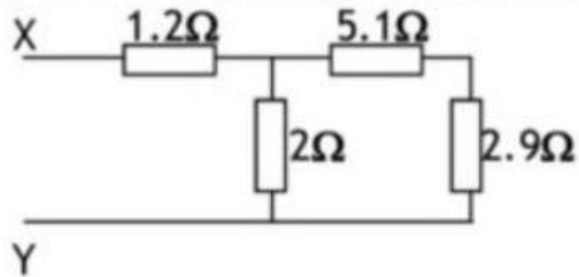- (a) Total resistance of the circuit. (4)
- (b) The current flowing in the 2.9Ω resistor. (4)
- (c) The potential difference across the 5.1Ω resistor. (2)



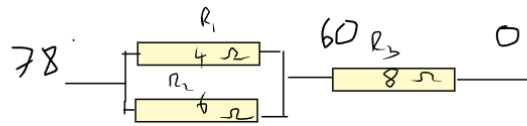Q8 March 2018
A 4 Ohm resistor is connected in parallel with a 6 Ohm resistor, and this combination is connected in series with an 8 Ohm resistor. The current flowing through the 8 Ohm resistor is 7.5 Amps. Calculate EACH of the following:
(a) The applied voltage; (4)
(b) The current in EACH of the parallel resistors. (4)



Circuit Current = 7.5 Amp

a) Resistance over Parallel section

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{6}$$

$$\frac{1}{R_T} = \frac{5}{12}$$

$$R_T = 2.4 \Omega$$

Resistance over Series Section

$$R_T = R_4 + R_3$$

$$R_T = 2.4 + 8 = 10.4$$

Voltage

$$V = I \times R = 7.5 \text{ volts}$$



b) R_3 $V = 60$

$$I = 7.5$$

$$R = 8$$

Voltage over Parallel section = 18



$$V = 18$$

$$I = 4.5 \text{ A}$$

$$R = 4$$



$$V = 18$$

$$I = 3 \text{ Amps}$$

$$R = 6$$

Q9 December 2019


A battery has an e.m.f. of 38 volts and an internal resistance of 4 ohms. It feeds a circuit consisting of three resistors connected in parallel. The resistors have values of 10 ohm, 20 ohm and 30 ohm.

Calculate EACH of the following:

(a) the battery terminal voltage;

(4)

(b) the current in EACH resistor.

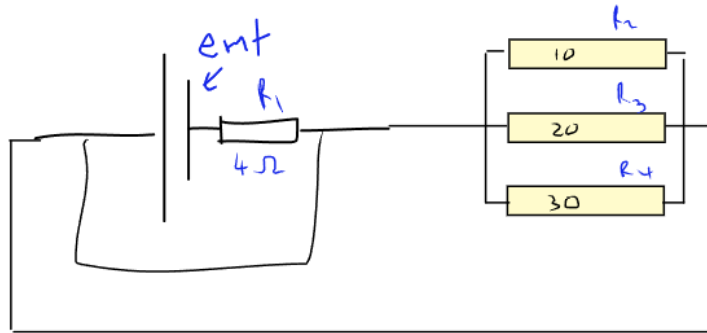

Resistance over parallel section

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} = \frac{11}{60}$$

$$R_T = \frac{60}{11} = 5.4545 \Omega$$

Circuit Resistance (series)

$$R_T = 4 + 5.4545 = 9.45$$

Circuit Current

$$I = \frac{V}{R} = \frac{38}{9.4545} = 4.019 \text{ Amp}$$

Voltage drop over R1

$$V = IR$$

$$V = 4.019 \times 4$$

$$V = 16.0769$$

Terminal voltage

$$38 - 16.0769 = 21.923 \text{ Volts}$$

U
I R


$$I_2 = \frac{V}{R_2} = \frac{21.9}{10} = 2.19 \text{ A}$$

$$I_3 = \frac{V}{R_3} = \frac{21.9}{20} = 1.095 \text{ A}$$

$$I_4 = \frac{V}{R_4} = \frac{21.9}{30} = 0.73 \text{ A}$$

$$I_1 = \frac{16.0764}{4} = 4.01911 \text{ A}$$

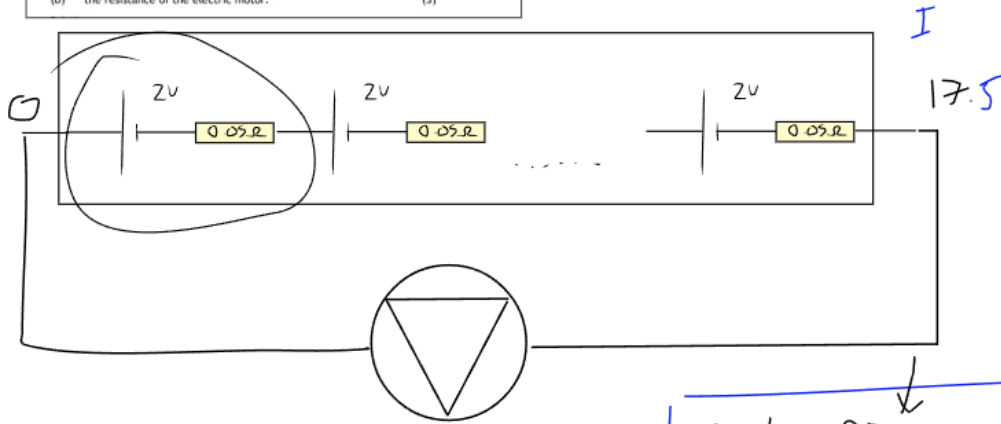Q9 March 2017
 A battery consists of 10 cells connected in series, each cell having an e.m.f. of 2V and an internal resistance of 0.05Ω. The battery supplies a current of 5A to an electric motor.
 Calculate each of the following:
 (a) the potential difference of the battery; (5)
 (b) the resistance of the electric motor. (3)



Motor
 $V = 17.5 \text{ V}$
 $I = 5$
 $R = 3.5 \Omega$

Circuit current = 5 A
 Resistance in battery = $0.05 \times 10 = 0.5$

$$E_{mf} = PD \text{ on battery} + IR$$




$$PD = E_{mf} - \underbrace{I \times R}_{\substack{\text{Voltage used} \\ \text{by internal} \\ \text{resistance}}} \\
17.5 = 20 - 5 \times 0.5 \\
2.5$$

$$PD = E_{mf} - IR \\
17.5 = 20 - 2.5$$

17.5V


Q8 December 2016
A battery of EMF 12V and internal resistance 0.2Ω is connected across the terminals XY of the circuit shown. Calculate EACH of the following:

(a) Total resistance of the circuit. $= 3\Omega$ (4)
 (b) The current flowing in the 2.9Ω resistor. (4)
 (c) The potential difference across the 5.1Ω resistor. (2)

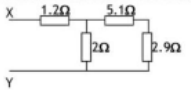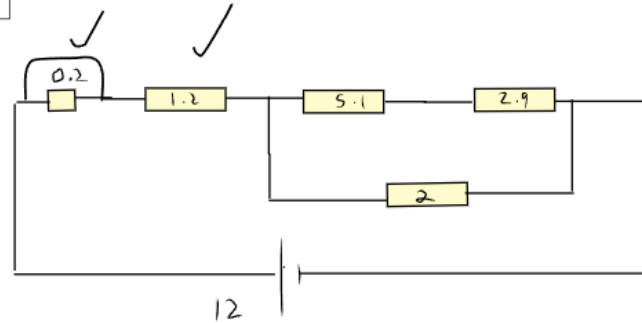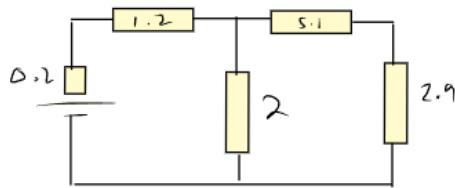Resistor in Series


$$R_T = 5.1 + 2.9 = 8\Omega$$

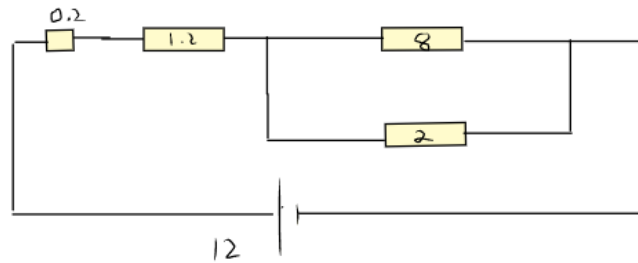

Resistor in Parallel

$$\frac{1}{R_T} = \frac{1}{8} + \frac{1}{2} = \frac{5}{8}$$


$$R_T = \frac{8}{5} = 1.6$$

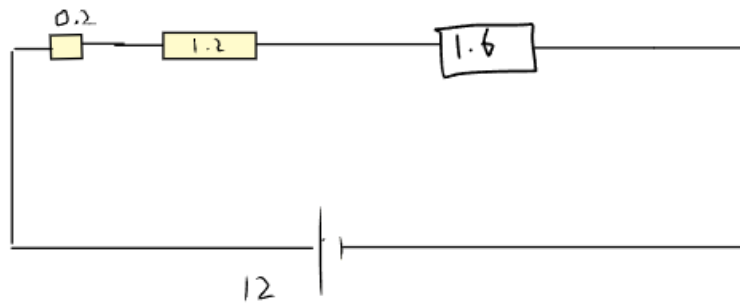

Resistors in Series

$$R_T = 0.2 + 1.2 + 1.6$$

$$R_T = 3$$

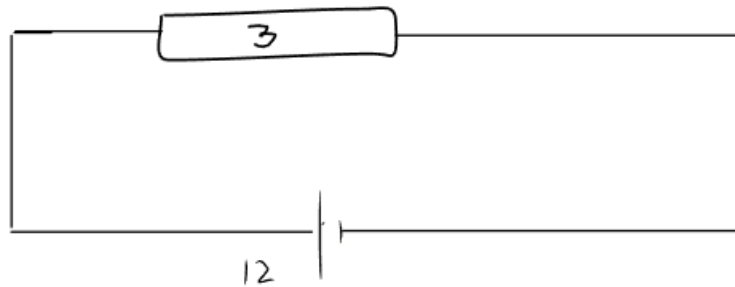


$$R = 3$$

$$V = 12$$

$$I = \frac{12}{3} = 4 \text{ Amps}$$

$$V$$
$$I R$$


Circuit

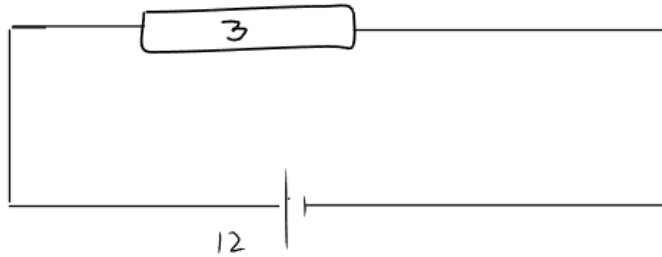

$$V = 12$$

$$I = 4$$

$$R = 3$$

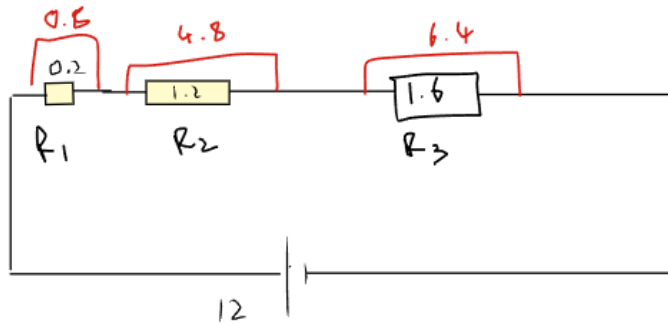

Series = Voltage drops across components




$$R_1 = \begin{matrix} V = 0.8 \\ I = 4 \\ R = 0.2 \end{matrix}$$

$$R_2 = \begin{matrix} V = 4.8 \\ I = 4 \\ R = 1.2 \end{matrix}$$
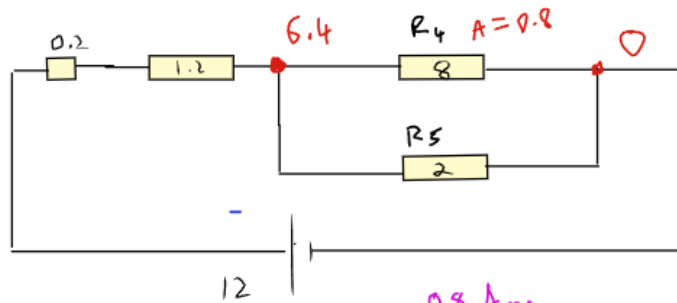
$$R_3 = \begin{matrix} V = 6.4 \\ I = 4 \\ R = 1.6 \end{matrix}$$






Current over parallel section

R_4 $V = 6.4$
 $I = 0.8$
 $R = 8$

$I = \frac{V}{R}$

R_5 $V = 6.4$
 $I = 3.2$
 $R = 2$

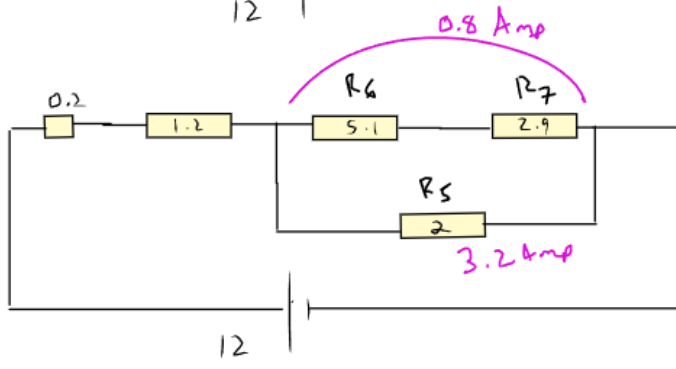

Series section

(Voltage drops)

R_6 $V = 4.08$
 $I = 0.8$
 $R = 5.1$

$V = I \cdot R$

R_7 V
 $I = 0.8$
 $R = 2.9$

